

# MMIC Chip Design

---

EERF – 6396

Prof. Dr. Randall E. Lehmann  
Dept. of Electrical Engineering  
The University of Texas at Dallas

Submitted by: Omkar Kulkarni

11/20/2017

## 1. Introduction

**Objectives: Design two Butterworth High Pass Filters:**

- Ideal (lumped element) HPF
- MMIC HPF of GaAs

## 2. Design

- PART – 1: Ideal (lumped element) HPF**

Parameter	Design Goal
$f_c$ (GHz)	10.0
Rejection at 5GHz (dB)	$\geq 30$
No. of elements (N, odd)	Minimum
Pi topology	
$Z_G$ and $Z_L = 50\Omega$	

- From the attenuation behavior chart the number of elements chosen to achieve the desired attenuation is 7.
- Coefficients for N = 7 Butterworth are:

7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450	1.0000
---	--------	--------	--------	--------	--------	--------	--------	--------

- Calculating the Values:


$$L_1 = L_7 = \frac{R}{2\pi \times f_c \times g_n} = \frac{50}{2\pi \times 10G \times 0.445} = 1.788 \text{ nH}$$

$$C_2 = C_6 = \frac{1}{2\pi \times R \times f_c \times g_n} = \frac{1}{2\pi \times 10G \times 50 \times 1.247} = 0.2552 \text{ pF}$$


$$L_3 = L_5 = \frac{R}{2\pi \times f_c \times g_n} = \frac{50}{2\pi \times 10G \times 1.8019} = 0.4416 \text{ nH}$$

$$C_4 = \frac{1}{2\pi \times R \times f_c \times g_n} = \frac{1}{2\pi \times 10G \times 50 \times 2} = 0.1591 \text{ pF}$$

- **Schematic**

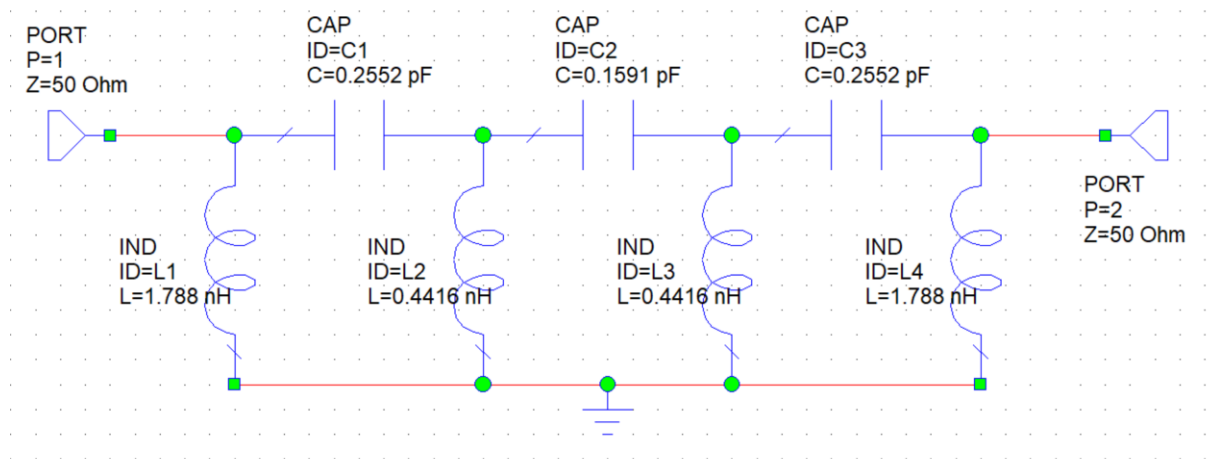

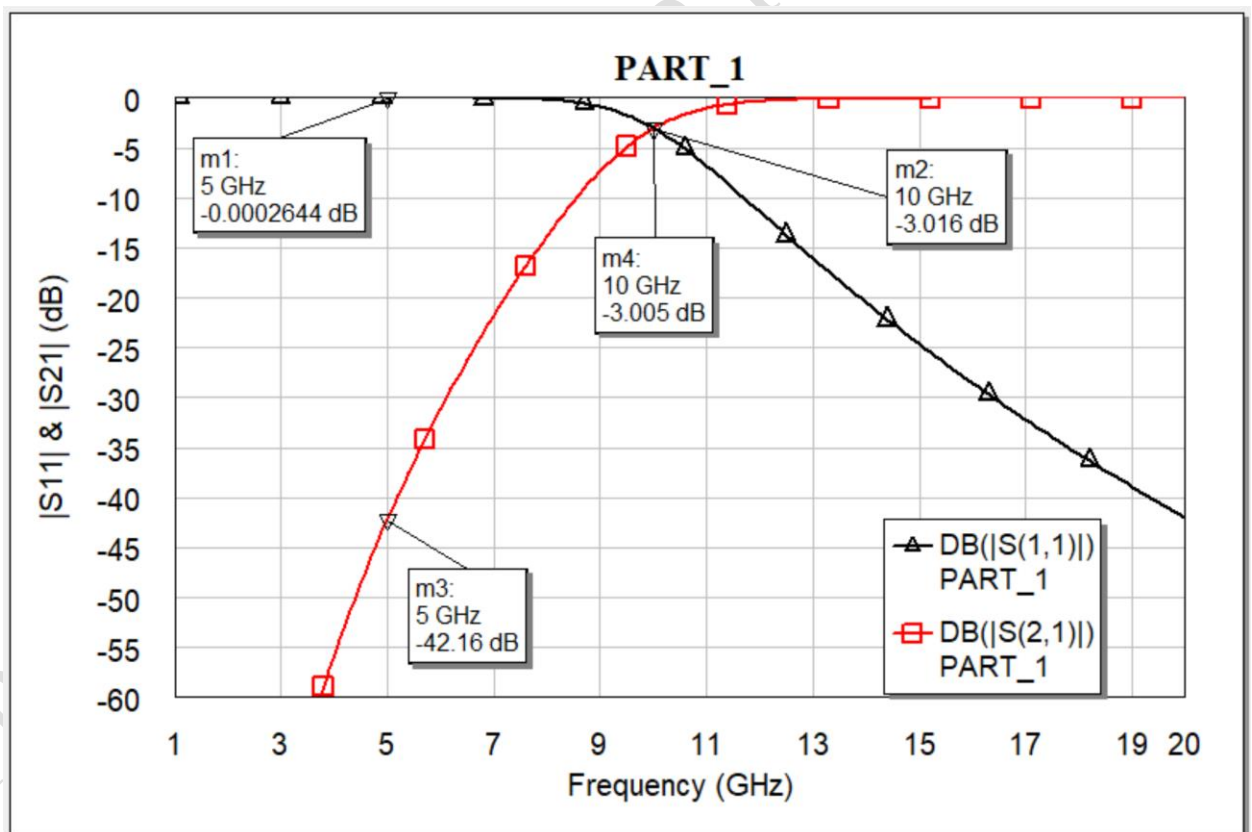- **S-parameters from circuit simulations**



- **Compliance Matrix:**

Parameter	Design Goal	Simulated Performance	Compliant (Yes/No)
$f_c$ (GHz)	10	10	Yes
Rejection at 5GHz (dB)	> 30	42.16	Yes

**Summary:** The results exceed the required specifications with  $N = 7$ . We will design the next part with  $N = 5$ .

**b. PART – II: MMIC HPF on GaAs**

Parameter	Design Goal
$f_c$ (GHz)	10.0
Rejection at 5GHz (dB) (actual $ S_{21} $ )	$\geq 25$
No. of elements (N, odd)	Minimum
Tee topology	
$Z_G$ and $Z_L = 50\Omega$	
MMIC Chip Size (sq. mm)	Minimum

1. Butterworth coefficients for  $N = 5$ :

5	0.6180	1.6180	2.0000	1.6180	0.6180	1.0000
---	--------	--------	--------	--------	--------	--------

2. Calculating the values:

T topology is chosen to minimize the number of inductors which would save chip area.


$$C_1 = C_5 = \frac{1}{2\pi \times R \times f_c \times g_n} = \frac{1}{2\pi \times 10G \times 50 \times 0.6180} = 0.515 \text{ pF}$$

$$C_3 = \frac{1}{2\pi \times R \times f_c \times g_n} = \frac{1}{2\pi \times 10G \times 50 \times 2} = 0.5 \text{ pF}$$


$$L_2 = L_4 = \frac{R}{2\pi \times f_c \times g_n} = \frac{50}{2\pi \times 10G \times 1.618} = 0.4918 \text{ nH}$$

### 3. Realizing the L and C on GaAs substrate:

 
- i. AWR MESFET library is used to streamline the MMIC design process
- ii. MSUB is defined as follows:



 - iii. TFCM element is used for capacitors: TFCM shows the calculated capacitance in green for the set parameters. Adjusting the values of width, length the required C values are achieved. The length of all capacitors is kept constant and the width is tuned which further helped in reducing the x dimension.




 - iv. MCINDS element is used for inductors:  $Z_{\text{IN}}$  was plotted on smith chart to achieve the required  $X_L$  at 10 GHz by tuning radius, width, number of turns, length of the bridge and spacing.




- v. Appropriate connecting elements are added to make a practically realizable layout.
- vi. TVIA are used to connect the inductors to the ground plane and GSG pads are added for auto-probing capability on both sides.
- vii. Tuning was done as necessary to compensate for the connecting elements.

• **Schematic:**

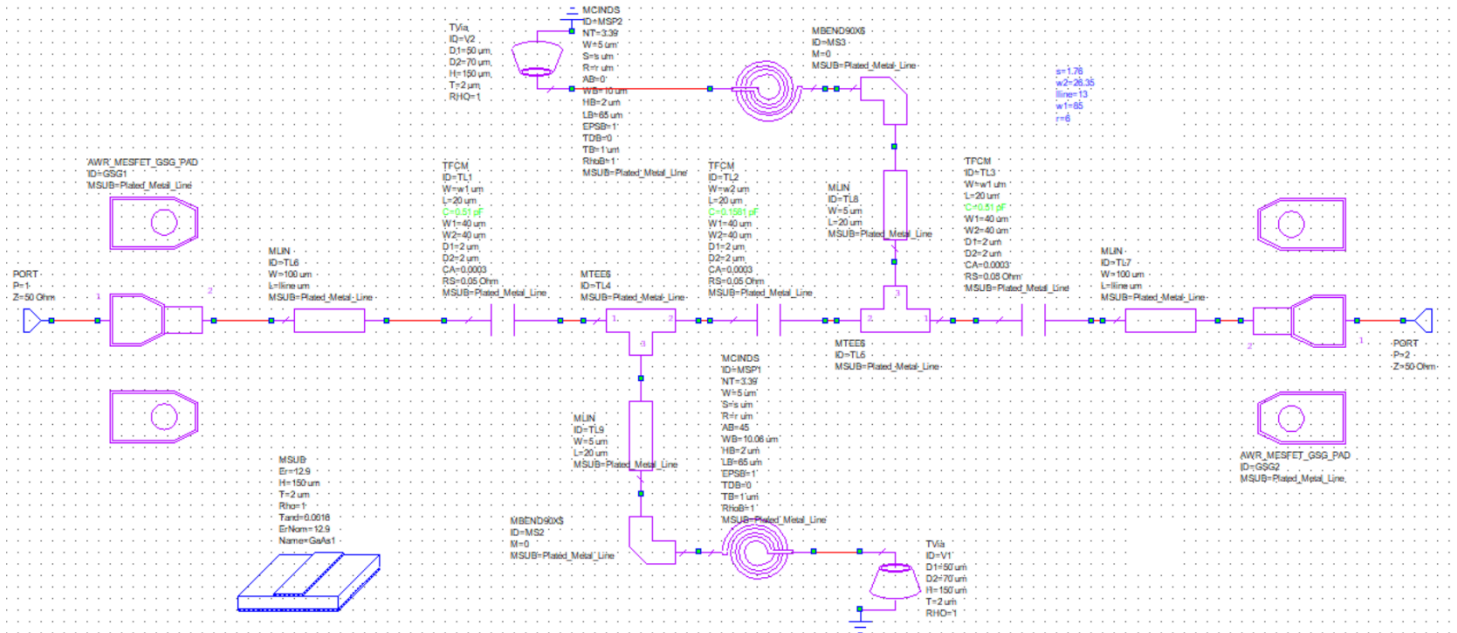


• **Layout:**

 


All dimensions in micrometer

- **3-D Layout:**

 

- Measurements:

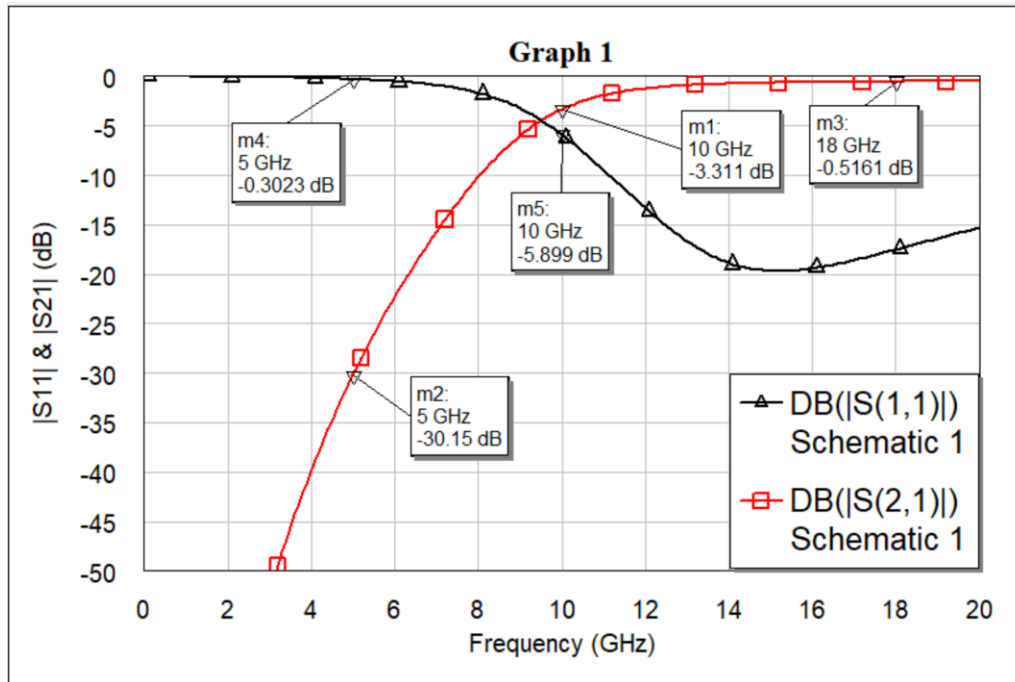


- Compliance Matrix:

Parameter	Design Goal	Simulated Performance	Compliant (Yes/No)
$f_c$ (GHz)	10	10	Yes
Rejection at 5GHz (dB)	>25	30.15	Yes



- **MMIC yield**

- Area of 1 chip:

 

Leaving a margin of 25  $\mu\text{m}$  from all 4 sides:

Length =  $460 + 25 + 25 = 510 \mu\text{m}$


Width =  $509 + 25 + 25 = 559 \mu\text{m}$

Total area of unit chip = Length  $\times$  Width =  $0.510 \text{ mm} \times 0.559 \text{ mm} = \mathbf{0.285 \text{ mm}^2}$

- Calculating the available wafer area:

Wafer diameter = 150 mm; wafer radius = 75 mm

Discounting the outer 10 mm:

 

Remaining area =  $\pi r^2 = \pi \times 65^2 = 13273 \text{ mm}^2$

Discounting 5% area for PCM chips =  $13273 \times 0.95 = 12609.56 \text{ mm}^2$

Considering the total process and RF yield of 90% =  $12609.56 \times 0.90 = \mathbf{11348.6 \text{ mm}^2}$

$$\text{- Expected yield} = \frac{\text{Available wafer area}}{\text{Unit chip area}} = \frac{11348.6}{0.285} = \mathbf{39816}$$

**Summary:** The MMIC HPF has a cutoff frequency of around 10 GHz with rejection of 30.15 dB at 5 GHz. Around 39800 chips can be expected from a 150 mm diameter GaAs wafer.